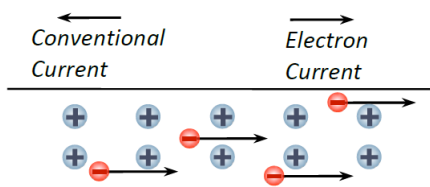


14 Current of Electricity

Electric Current



The **charge** that passes through a given point is the product of the steady current flowing past the point and the time during which the current flows, i.e. $Q = It$ [unit: Coulomb (C)]

If current is not constant, the amount of charge can be found by finding the area under the current-time graph, i.e. $Q = \int I \cdot dt$.

Important formula: $I = nAV_dq$ (given but need to know how to derive) where n is the number density of charges per unit volume, A is the cross-sectional area, V_d is the drift velocity and q is the charge on the carrier.

Potential Difference

The **potential difference** (p.d.) between two points is the amount of electrical energy converted to other forms of energy per unit charge flow between the points, i.e. $V = \frac{W}{Q}$ Given that $W = \text{Power} \times \text{time}$ and $Q = It$, $V = \frac{P}{I}$

Resistance and Resistivity

The **resistance** R of a conductor is defined as the ratio of the p.d. V across it to the current I through it, i.e. $R = \frac{V}{I}$ [unit: ohm (Ω)]
Combining the equations $P = IV$ and $V = IR$, we can obtain $P = I^2R$ and $P = \frac{V^2}{R}$.

Determining Resistance

At a given temperature, the **resistance** R of a conductor is determined by $R = \rho \frac{L}{A}$.

I-V Characteristic Graphs

Ohm's Law: the current flowing through a metallic conductor is directly proportional to the p.d. V between its ends, provided that all other physical conditions are kept constant.

The resistance R of an ohmic conductor such as a metallic conductor at constant temperature is constant since $\frac{V}{I}$ is constant.


Non-ohmic conductors: filament lamp, semiconductor diode, thermistor

Sources of Electromotive Force

The **electromotive force** (e.m.f.) of a source is the energy converted into electrical energy from other forms per unit charge in driving charges round a complete circuit, i.e. $E = \frac{W}{Q}$.


In practice though, the source has **internal resistance** r and thus not all electrical energy generated is available to the external load R .

Terminal Potential Difference

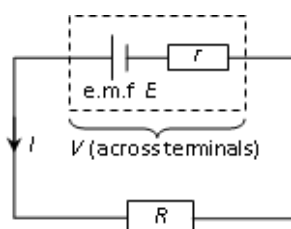

The terminal p.d. is equal to the sum of the e.m.f. and potential drop across internal resistance r , and to p.d.

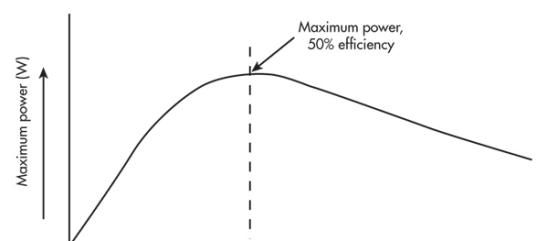across external resistance R , i.e. $V = E - Ir = IR$



Maximum power theorem: A given source of e.m.f. delivers the maximum amount of power to a load when $R = r$.